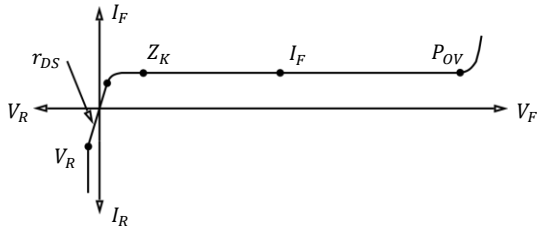


Application Note : JFET Implementations

The Current Regulator Diode is a JFET with the Gate tied to the Source and operating in the saturation region of the characteristic curve as seen in Figure 1.




In the saturation region, the current output is very constant over a wide range of Supply Voltages. With the Drain Voltage well centered in the saturation region, noise on the voltage source will not cause changes in the regulated output current.

Low current, Current Regulator Diodes (CRDs) are good for sourcing or sinking supply current for sensors, differential input stages, and other electronic components that are depending on a steady current source. Larger CRDs are also good for powering LEDs and LED arrays that are on or off together like a break light in a car, warning signs, control panel indicators or ambient lighting just to name a few.

The CRD series of Current Regulator Diodes by InterFET have a unique feature; the Gate lead is brought out of the device and tied to the Source externally to increase the capabilities of the CRD. With the Gate lead on a separate pin from the Source, the device can be turned on and off like an analog switch. When a negative voltage is applied to the Gate lead ($V_{GS(OFF)}$), the current flowing through the device will go to zero.

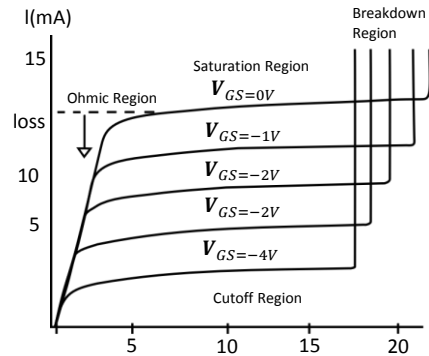Another application for the Gate lead is to change the amount of current flowing through the device. In Figure 2, as the Gate Voltage (V_{GS}) goes more negative, the entire current output curve moves lower. This can be used to dim the LED output. The output change can be gradual or instantaneous with immediate stability.



The CRD will protect against surge currents as well as voltage fluctuations and because it is based on a JFET design, there is extremely low injected noise.


Another interesting characteristic of CRDs is that they can be biased to achieve near zero temperature-coefficient performance over a wide temperature range. As the temperature increases, the mobility of the majority carriers within the channel is inhibited, about $0.8\%/^{\circ}\text{C}$. Any reverse-biased PN junction, in a CRD or bipolar Diode, exhibits a barrier-potential depletion width that decreases with increased temperature, at about $-2.2\text{mV}/^{\circ}\text{C}$.

For the CRD, this near zero temperature-coefficient can be realized if the channel conductance decreases cause the drain current to decrease, and the gate-to-channel barrier potential decreases causing the drain current to increase at the same rate to offset each other. It turns out that the near zero temperature-coefficient can be achieved when the Gate-Source Voltage is equal to **0.63V less** than the Gate-Source **Cutoff Voltage**. ($V_{GS} = V_{GS(off)} - 0.63\text{ V}$)


In addition to applications with varying temperatures, the CRD is also very well suited for demanding temperature extremes. The CRD has also performed well in high radiation environments.



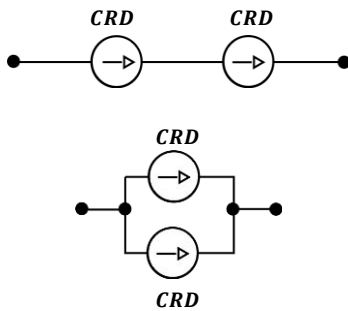
Disclaimer: It is the Buyers responsibility for designing, validating and testing the end application under all field use cases and extreme use conditions. Guaranteeing the application meets required standards, regulatory compliance, and all safety and security requirements is the responsibility of the Buyer. These resources are subject to change without notice.



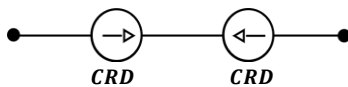
The Current Regulator Diodes (CRDs) will evenly split the load across multiple devices to increase the Voltage or Current carrying capability. By adding CRDs in series and parallel both the current carrying, and the breakdown voltage capability can be increased.



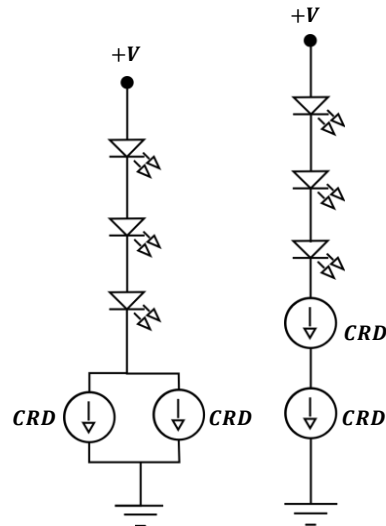
The current flow will be limited by the CRD in that direction while the CRD in the opposite direction will pass the current through.



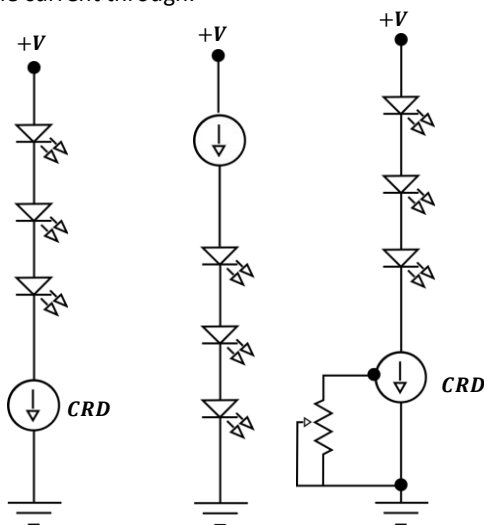Driving LEDs that require higher current or higher voltage can be accomplished by stacking CRDs in series or parallel since they will share the load naturally by design.




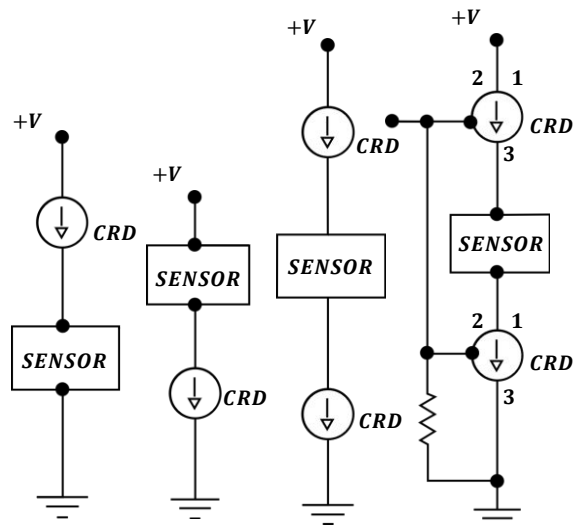The maximum number of LEDs is determined by adding the voltage drop across the LEDs and the CRD. Add the current requirements for each LED to select the correct CRD from the data sheet.




By using a CRD to bias your sensors, it is possible to reduce the noise and increase the accuracy of your sensor, especially in a noisy electrical environment. The CRD will also act as an Analog Switch.

Common Source

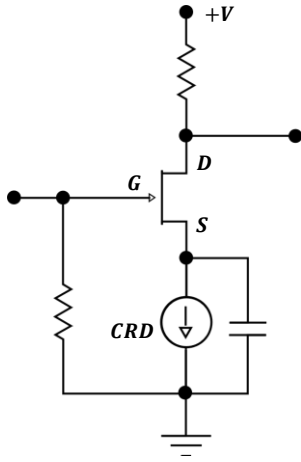


Source Follower

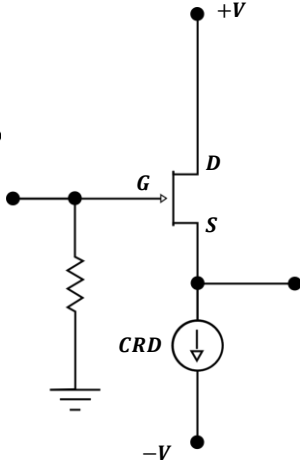


Transistor performance can be improved by the stable, well defined dc bias point.

Constant-Current Self Biased Source-Follower:

With Improved Stability

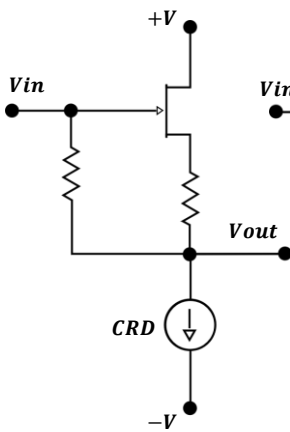


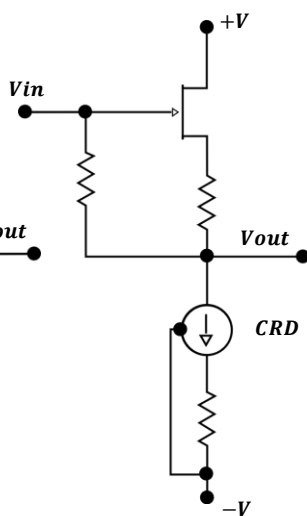With Zero-Temperature Coefficient Operation



When the resistor values are selected properly to allow operation at about $V_{GS} = V_{GS(off)} - 0.63 \text{ V}$ for the CRD and $V_P + 0.7 \text{ V}$ for the JFET, the circuit will have a near Zero-Temperature Coefficient (Zero-TC). This means that the device will vary minimally with changes in temperature.

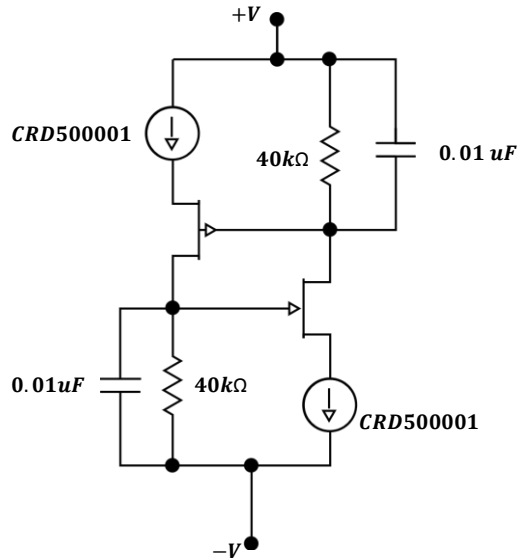Cascode 200 uA Floating Current Source, Regulation (15V – 30V) is 0.00005%/V



This Cascode floating current source will regulate 15-30V to 0.00005%/V supplying 200uA. The output impedance will appear to be 10 GΩ. The low voltage compliance is limited by the combination of the gate reference voltages to around 8V. The high voltage compliance is limited by the lower voltage rated JFET.